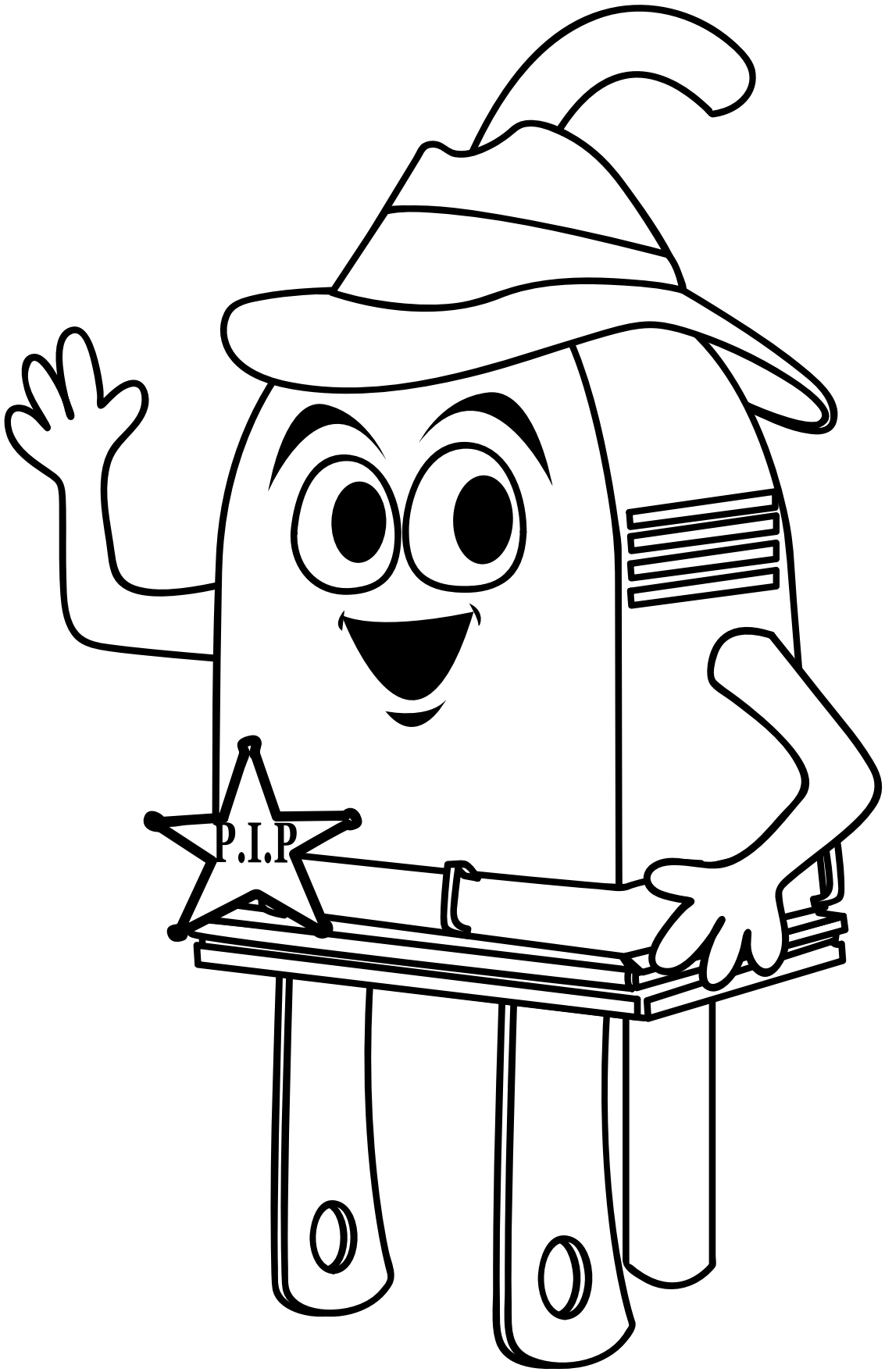
P.I.P

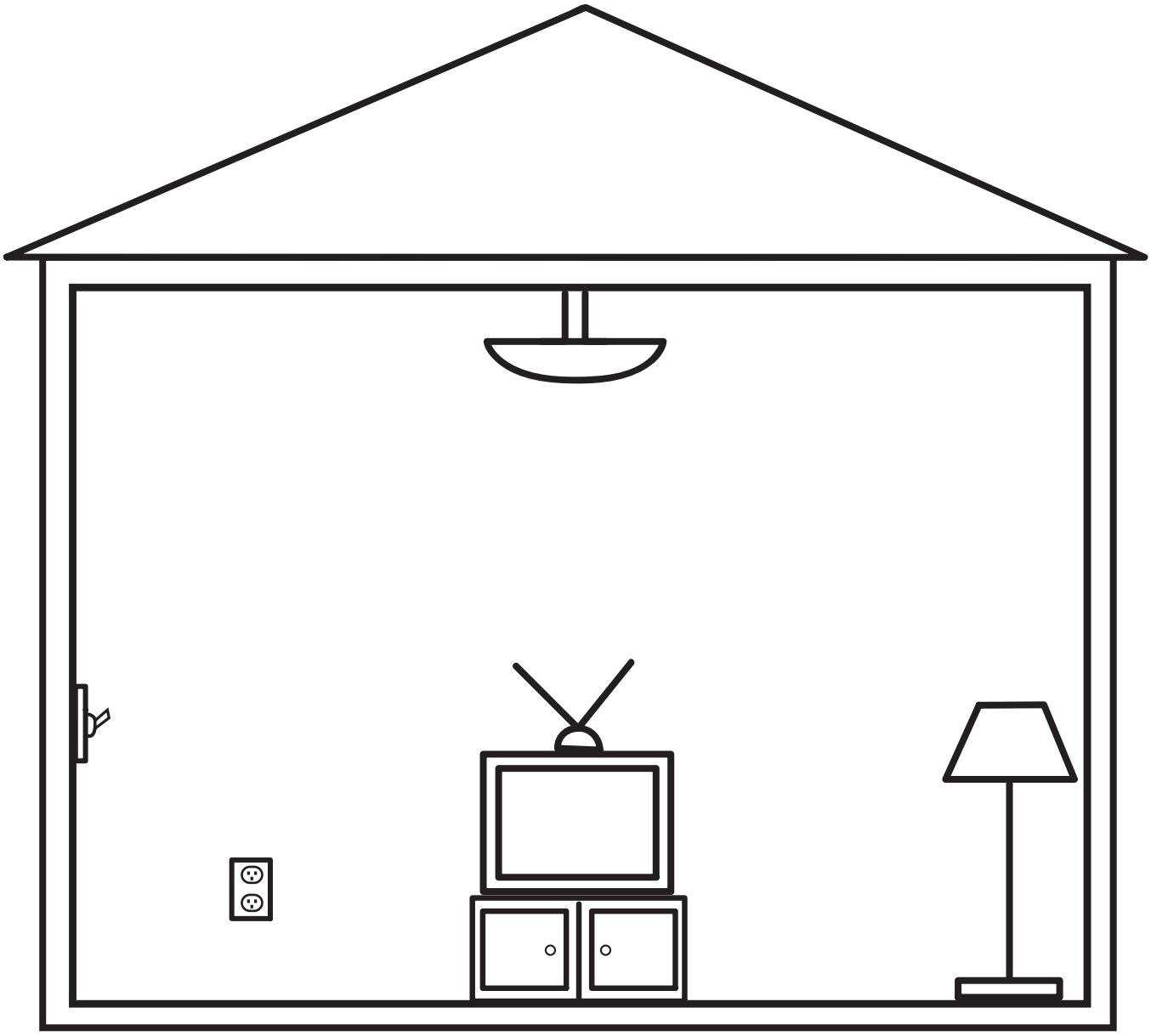

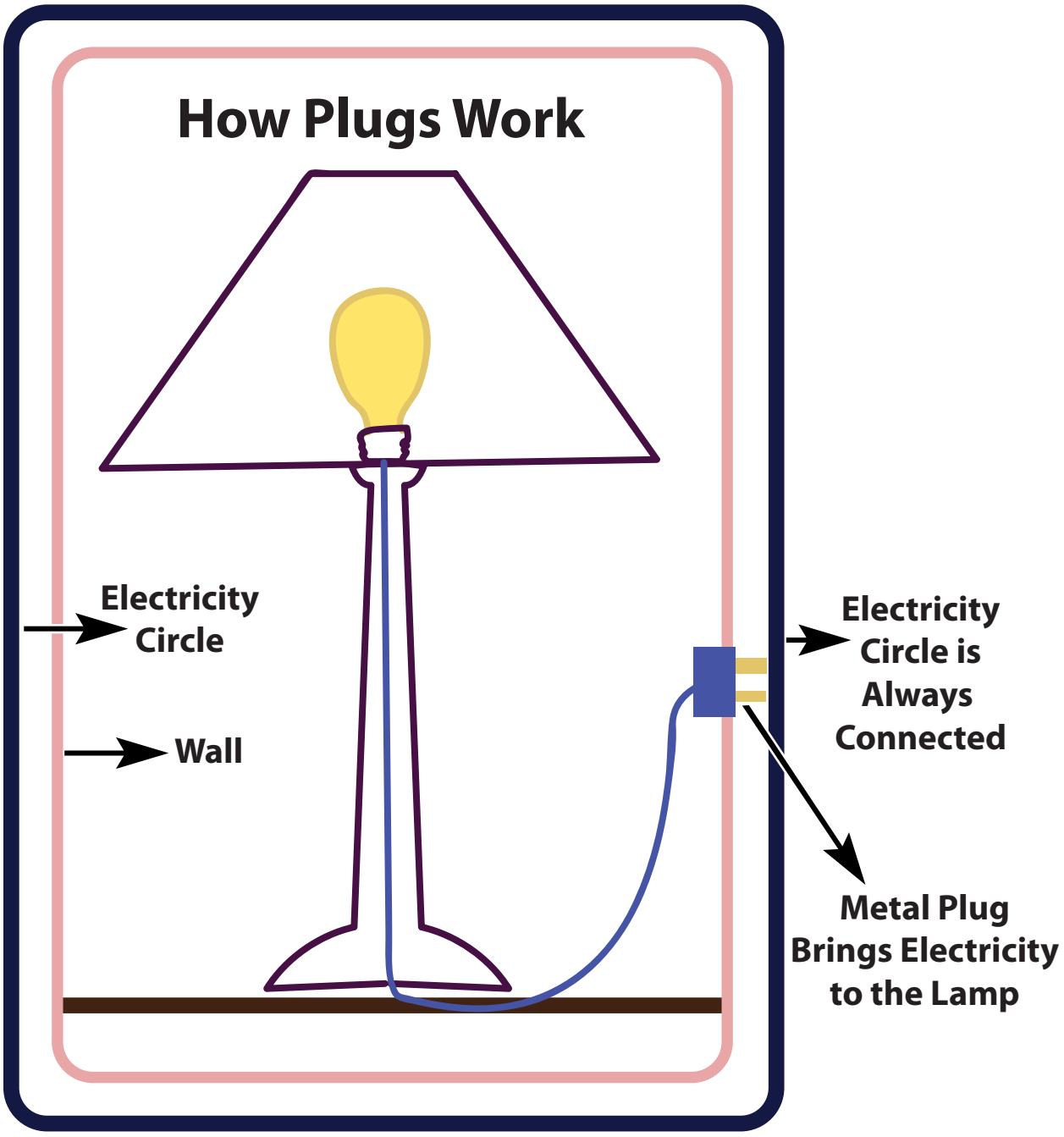
How Plugs Work
Electricity Circle
Wall
Electricity Circle is Always Connected
Metal Plug Brings Electricity to the Lamp

How Switches Work: ON

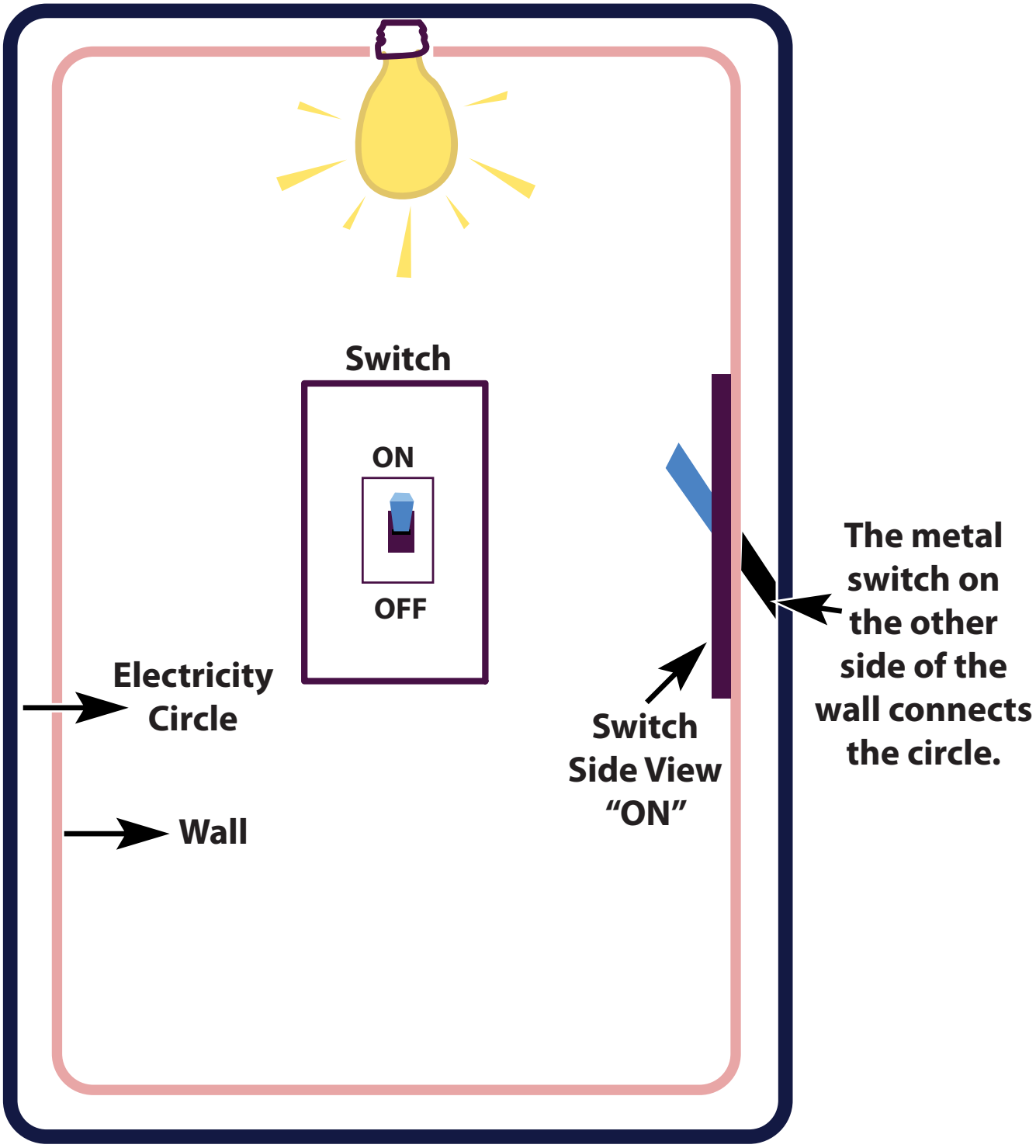
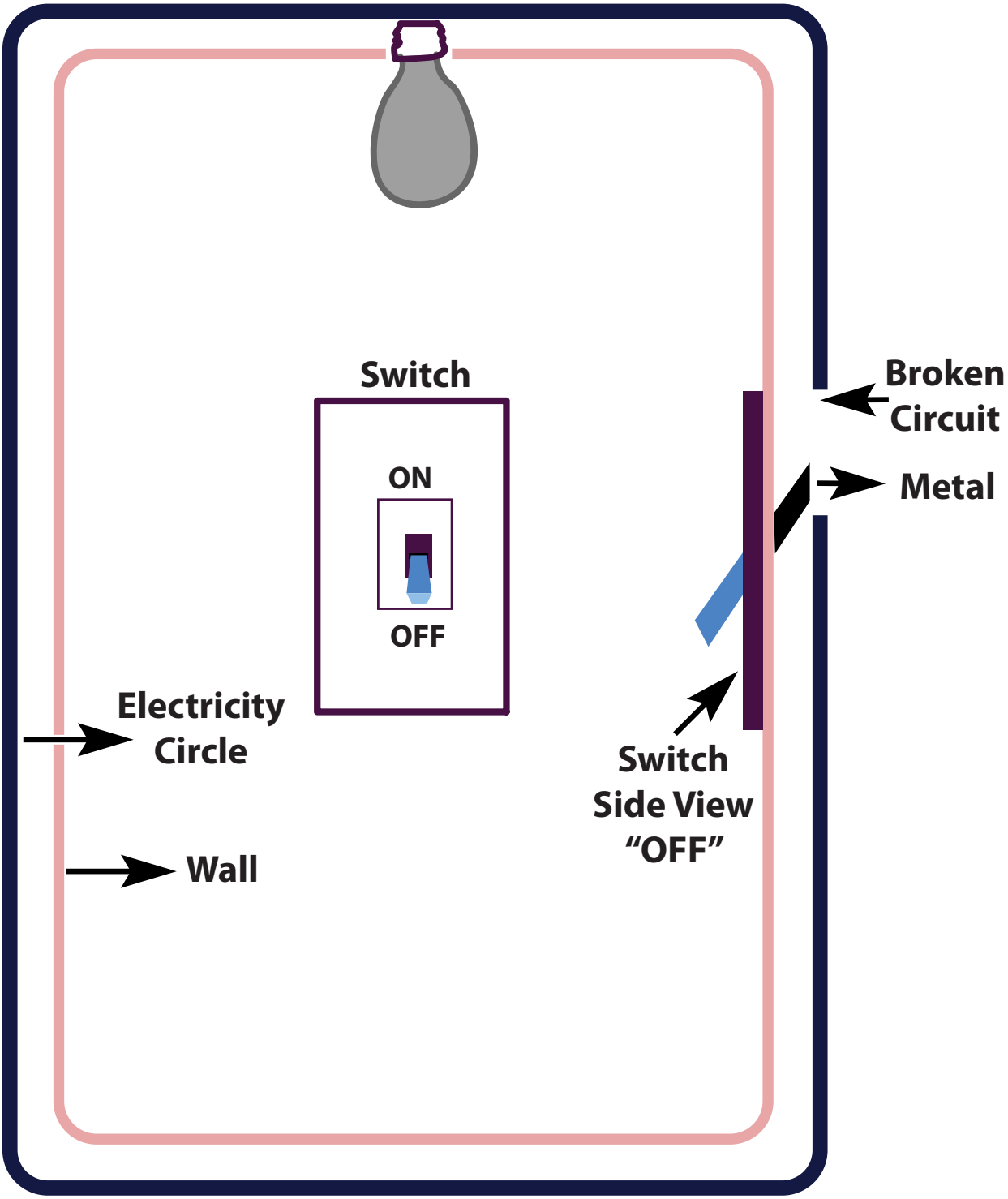
How Switches Work: OFF